

**Credit Based First Semester B.C.A. Degree  
Examination, Nov./Dec. 2018  
COMPUTER ORGANIZATION  
(Common to All Batches)**

Time : 3 Hours

Max. Marks : 80

**Note :** Answer **any ten** questions from Part – A and **any one full** question **each** Unit of Part – B.

## PART – A

1. a)  $(11110001101)_2 = ( )_8$ . (2×10=20)
- b) Write 9's and 10's complement
  - i)  $(701189)_{10}$
  - ii)  $(4706.15)_{10}$
- c) Write the Logic Symbol and truth table of XOR gate.
- d) Write the general structure of 2 and 3 variables K-Map.
- e) Prove that  $ABC + A'B + ABC' = B$ .
- f) Write the dual of the given expression  $F = (X + Y)(X + Y' + Z)$
- g) Write the logical expression for 1 bit comparator.
- h) Write the truth table of Half Subtractor.
  - i) Write the truth table of octal to binary encoder.
  - j) Write the excitation tables of SR and T flip flop.
- k) Draw a block diagram of 4 bit Right Shift bit register using D flip-flop.
- l) Define counter. How many flip-flops are required to design MOD-18 synchronous counter ?



## PART – B

## Unit – I

2. a) Perform following Conversion :

i)  $(351)_8 = ( )_{10}$

ii)  $(785)_{10} = ( )_8$

iii)  $(BCA)_{16} = ( )_2$

b) Perform the following subtraction using 9's and 10's complement :

i)  $(216)_{10} - (485)_{10}$

ii)  $(1024)_{10} - (925)_{10}$

c) State the postulates of Boolean algebra.

**(5+5+5)**

3. a) Perform following Conversion :

i)  $(ABCD.65)_{16} = ( )_2$

ii)  $(785)_{10} = ( )_8$

iii)  $(1101)_2 = ( )_{10}$

b) Perform the following subtraction using 1's and 2's complement.

i)  $(1101)_2 - (1000)_2$

ii)  $(1011)_2 - (1100)_2$

c) State and prove any five theorems of Boolean algebra.

**(5+5+5)**

## Unit – II

4. a) Express the Boolean function  $F(A, B, C) = A' + BC$  as sum of minterm and product of maxterm.

b) Prove that NAND is universal gate.

c) Using K-Map simplify the following expression :

$$F(w, x, y, z) = \sum(1, 3, 4, 5, 6, 7, 9, 11, 12, 13, 14, 15).$$

**(5+5+5)**

5. a) Using K-Map simplify the following expression :

$$F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 14).$$

b) Implement the Boolean function  $F(A, B, C, D) = AB + C'D'$  using only NOR gate.

c) Express the Boolean function  $F(A, B, C) = (A' + B')(B + C)$  as sum of minterm and product of maxterm.

**(5+5+5)**

**Unit – III**

6. a) Explain the working of Full Adder.  
b) Explain the working of 3 to 8 line Decoder.  
c) Design BCD to Excess -3 code converter. (5+5+5)
7. a) Design 2 bit Magnitude Comparator.  
b) Design and explain BCD Adders.  
c) Explain the working of 2×4 De-Multiplexer. (5+5+5)

**Unit – IV**

8. a) Explain the working of clocked JK flip-flop. Write the characteristics and logical expression.  
b) Design 4 bit Binary ripple counter.  
c) Design BCD synchronous counter using T flip-flop. (5+5+5)
9. a) Explain state table, state diagram and state equation using example.  
b) Explain the working of Bi-directional shift register.  
c) Design a OCTAL Synchronous counter using JK flip-flop. (5+5+5)
-