



First Semester B.C.A. Degree Examination, April 2021
(Choice Based Credit System)
(2019 – 2020 Batch Onwards)
COMPUTER ORGANIZATION

Time : 3 Hours

Max. Marks : 80

Instruction : Answer **any ten** questions from Part – A and **one full** question from **each** Unit of Part – B.

PART – A**(10×2=20)**

1. a) Obtain the 9's and 10's complements of the following decimal number 341.23.
- b) Obtain the 1's and 2's complements of the binary number 1110101.
- c) Write excess-3 and binary equivalent of $(845)_{10}$.
- d) Draw the logic circuit for $F(X, Y, Z) = X'Y + X'Z$.
- e) How to write the complement of a Boolean function ? Also write the complement of $F(X, Y, Z) = X'YZ' + X'Y'Z$.
- f) Write the general structure of 3 and 4 variables K-Map.
- g) What is half subtractor ? Write its truth table.
- h) What is encoder ? Write the truth table of octal to binary encoder.
- i) Write the truth table of 2 to 4 line decoder.
- j) Draw the circuit diagram of SR latch using NOR gate.
- k) Write the excitation tables of T and JK flip flop.
- l) Draw the block diagram of a sequential circuit.

PART – B**Unit – I**

2. a) Perform following Subtraction

- i) $(8052)_{10} - (3250)_{10}$ using 9's complement.
- ii) $(6320)_{10} - (8659)_{10}$ using 10's complement.



- b) Prove the following theorems of Boolean algebra.
- $x + x = x$
 - $x + xy = x$.
- c) Perform following conversion.
- $(11100101.10)_2 = ()_8$
 - $(45.B3)_{16} = ()_2$
 - $(789)_{10} = ()_8$. (4+5+6)
3. d) State the postulates of Boolean Algebra.
- e) Perform following subtraction.
- $(1001)_2 - (1011)_2$ using 1's complement method.
 - $(10011)_2 - (1001)_2$ using 2's complement method.
- f) Perform following conversion.
- $(152.A1)_{16} = ()_{10}$
 - $(345)_8 = ()_2$
 - $(915)_{10} = ()_{16}$. (5+4+6)

Unit – II

4. g) Using K-Map simplify the following expression.
 $F(w, x, y, z) = \sum(8, 9, 10, 11, 12, 13, 14)$.
- h) Express the Boolean function $F(A, B, C) = A + B'C$ as sum of minterm and product of maxterm.
- i) Prove that NAND is universal gate. (5+5+5)
5. j) Implement the Boolean function $F(A, B, C, D) = D(A + B) + CD'$ using only NOR gate.
 Draw the logic circuit for $F(X, Y, Z) = XY + X'Z$ using basic gates.
- k) Minimize $F(A, B, C, D) = \sum(0, 3, 4, 7, 8) + \sum d(10, 11, 12, 13, 14, 15)$ using K-Map. (5+5+5)

Unit – III

6. l) Explain the working of full adder.
- m) Design BCD to Excess-3 code converter.
- n) Explain the working of 3*8 Decoder. (5+5+5)



- 7. o) Design 2 bit magnitude comparator.
- p) Design and explain BCD adder.
- q) Explain the working of 4*1 multiplexer. (5+5+5)

Unit – IV

- 8. r) Explain the working of clocked SR flip flop.
 - s) Design a octal synchronous counter using JK flip flop.
 - t) Design 4 bit Binary ripple counter. (5+5+5)
 - 9. u) Design BCD synchronous counter using T flip flop.
 - v) Explain the working of bi-directional shift register.
 - w) Explain state table, state diagram and state equation using example. (5+5+5)
-