

Reg. No.

--	--	--	--	--	--	--	--	--	--

BCACAC 108

Credit Based First Semester B.C.A. Degree Examination, Oct./Nov. 2014
(New Syllabus) (2012-13 Batch Onwards)
COMPUTER ORGANIZATION

Time : 3 Hours

Max. Marks : 80

Note : Answer **any ten** questions from Part A and answer **any one full** questions from **each** Unit in Part B.

PART - A

1. a) Write BCD and Excess-3 code of $(276)_{10}$. (2x10=20)
b) Write 1's and 2's complement of $(1011)_2$.
c) Differentiate combination and sequential circuits.
d) Write the truth table and graphic symbol of NAND gate.
e) Prove that $x + x'y = x + y$.
f) Write a table to show the minterms for three binary variables x, y and z.
g) Write dual of $F = AB' + C$.
h) What is a half adder ? Write truth table for the same.
i) Draw SR latch circuit using NOR gates.
j) Write the excitation table of JK flip-flop.
k) Write the diagram of 4 bit shift register using D-flip flops.
l) Define counter. State any one differences between synchronous counter and ripple counter.

PART - B

UNIT - I

2. a) Perform following conversions

- i) $(75.75)_{10} = (?)_2$
ii) $(BCA)_{16} = (?)_2$
iii) $(11011.11)_2 = (?)_8$
b) Perform following subtractions using 9's and 10's complement methods
i) $(3762-975)_{10}$ ii) $(5310 - 7642)_{10}$
c) State and prove any three theorems of Boolean Algebra. (5+4+6)

P.T.O.

