

Reg. No.

--	--	--	--	--	--	--	--	--	--

BCACAC 108

Credit Based I Semester B.C.A. Degree Examination, Nov./Dec. 2015
(Common to All Batches)
COMPUTER ORGANIZATION

Time : 3 Hours

Max. Marks : 80

Note : Answer **any ten** questions from Part – A and **one full** question from **each** Unit of Part – B.

PART – A

(2×10=20)

1. a) Find the 1's and 2's complements of the binary number 1010101.
- b) Define byte and nibble.
- c) Write Excess-3 and binary equivalent of $(45)_{10}$.
- d) Draw venn diagram for $xy + xz$.
- e) Prove that $x + x = x$.
- f) Write the truth table and logic diagram of XOR gate.
- g) What is meant by duality principle ? Write the dual of the given expression
 $F = (x + y) (x + y')$. $x \cdot y + x \cdot y'$
- h) What is combinational logic circuit ? Draw the block diagram.
- i) What is magnitude comparator ?
- j) What is multiplexer ? Why is it called data selector ?
- k) What is flip flop ? Write characteristic table of D-flipflop.
- l) Define characteristic table and excitation table.



PART - B

Unit - I

2. a) Write a note on ICs. (4+6+5)
- b) Perform the following subtraction using 9's and 10's complement method :
 $8052 - 3250$.
- c) State and prove Demorgan's theorems for two variables.
3. a) Perform the following conversion
- i) $(BCD.A1)_{16} = ()_{10}$
- ii) $(915.67)_{10} = ()_8$. (4+6+5)
- b) Perform following subtraction using 1's and 2's complement methods :
 $(100.01)_2 - (101.11)_2$.
- c) Write a note on error detection codes.

Unit - II

4. a) Using K-map, simplify the following expression : (5+5+5)
- $$F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14).$$
- b) Implement the Boolean function $F(A, B, C, D) = A(B + CD) + BC'$ using only NAND gate.
- c) Write the sum of minterm and product of maxterm for given expression.
 $F(X, Y, Z) = XY + X'Z$.
5. a) Minimize $F(A, B, C, D) = \sum(0, 3, 4, 7, 8) + \sum d(10, 11, 12, 13, 14, 15)$ and draw the logic diagram for minimized expression. (6+5+4)
- b) Implement Boolean function $F = x'y'z + x'yz + yz'$ with basic gate and also write the truth table.
- c) Prove that NOR is a universal gate.



Unit – III

6. a) Explain the working of half adder with its logic diagram. (5+5+5)
b) Explain the working of 3×8 decoder.
c) Explain the working of 4×1 multiplexer.
7. a) Design 2 bit magnitude comparator. (5+5+5)
b) Design BCD to Excess-3 code convertor.
c) Design octal to binary encoder.

Unit – IV

8. a) What is shift register ? Explain with a neat diagram. (5+5+5)
b) Design 3-bit counter using JK flipflop.
c) Explain the working of clocked RS flipflop.
9. a) Explain state table, state diagram and state equation using an example. (5+5+5)
b) Design a 4-bit ripple counter.
c) Explain the working of JK flipflop. Write the characteristic table and characteristic equation.