

Reg. No.

--	--	--	--	--	--	--	--	--	--



BCACAC 108

**Credit Based First Semester B.C.A. Degree
Examination, October/November 2016
(Common to all Batches)
COMPUTER ORGANISATION**

Time : 3 Hours

Max. Marks : 80

Note : Answer **any ten** questions from Part – A and **any one full** question from **each** Unit of Part – B.

PART – A

1. a) Write the BCD and Excess-3 code of $(376)_{10}$. (10×2=20)
- b) Find the 1's and 2's complement of 10110.
- c) Write the algebraic function and graphic symbol of NOR gate.
- d) Prove that $x + xy = x$.
- e) Write the Venn diagram for $xy + yz$.
- f) What is principle of duality ? Write the dual of $X'Y + XY' = 1$.
- g) Write excitation table of JK flip flop.
- h) What is a half-subtractor ? Write its truth table.
- i) What is a register ? Write the block diagram of 4 bit register.
- j) What is BCD adder ?
- k) What is multiplexer ?
- l) Define :
 - i) State table
 - ii) State diagram.

P.T.O.



PART - B

Unit - I

2. a) Perform the following subtractions using 9's and 10's complement methods :
 i) $(8085 - 3250)_{10}$ ii) $(5310 - 7642)_{10}$
 b) Perform the following conversion : $(BCA.D)_{16} = (?)_2 = (?)_8 = (?)_{10}$
 c) State and prove DeMorgan's theorems for two variables. **(6+5+4)**
3. a) Perform the following subtraction using 1's and 2's complement methods :
 i) $10101 - 1011$ ii) $10110 - 11010$
 b) Perform the following conversion : $(915.67)_{10} = (?)_2 = (?)_8 = (?)_{16}$
 c) State any four postulates of Boolean algebra. **(6+5+4)**

Unit - II

4. a) Using K-Map simplify the following expression and draw the logic circuit for the simplified expression.
 $F(a, b, c, d) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
 b) Find the complements of :
 i) $F1 = XYZ' + X'Y'Z$ ii) $F2 = (A+B)'(A'+B'+C)(B+C)'$
 c) Prove that NAND is a universal gate. **(6+4+5)**
5. a) Write the truth table and logic circuit for the Boolean function $F = XY + X'Y + Y'Z$.
 b) Express the function $F(A, B, C) = B + A'C$ as sum of minterm and product of maxterm.
 c) Prove that NOR is a universal gate. **(5+5+5)**

Unit - III

6. a) What is a full-adder ? Explain its working.
 b) Design BCD to Excess-3 code converter.
 c) Explain the working of 4*1 multiplexer. **(5+5+5)**



- 7. a) Explain the working of BCD adder with block diagram.
- b) What is Magnitude Comparator ? Design a 1-bit Magnitude Comparator.
- c) Explain the working of 3x8 Decoder. (6+4+5)

Unit – IV

- 8. a) Explain the working of basic RS flip-flop using NOR gate.
 - b) Design 3 bit binary counter using JK flip flop.
 - c) What is a shift register ? Explain with a neat diagram. (5+5+5)
 - 9. a) Explain the working of basic JK flip-flop.
 - b) Design a mod 6 counter using T flip-flop.
 - c) Design a 4-bit binary ripple counter. (5+5+5)
-